

CENG2030 FUNDAMENTALS OF EMBEDDED SYSTEM DESIGN

LECTURE 4: CIRCUIT ANALYSIS

By Dr. Anthony Sum
Department of Computer Science and Engineering
The Chinese University of Hong Kong



1

CONTENTS

- Common Electronic Components
- Ohm's Law
- KCL & KVL
- Voltage & Current Divider




2

COMMON ELECTRONIC COMPONENTS

- Resistor
- Capacitor
- Inductor

- Diode
- Transistor
- Voltage Regulator

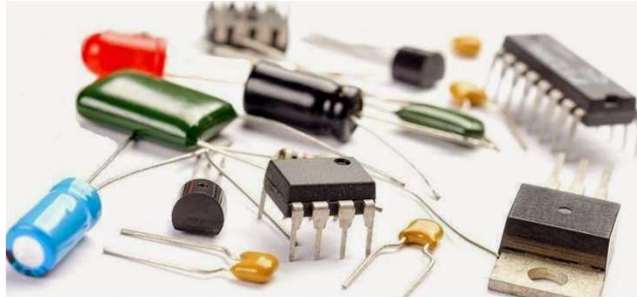


3


3

RESISTOR

- Resistor

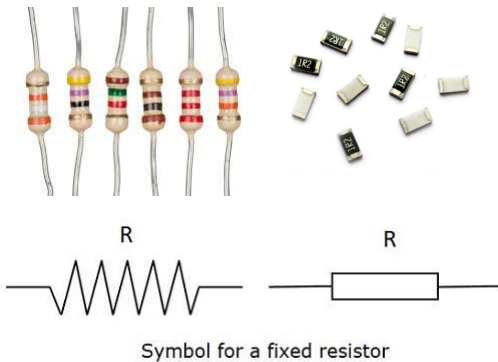

- Variable Resistor

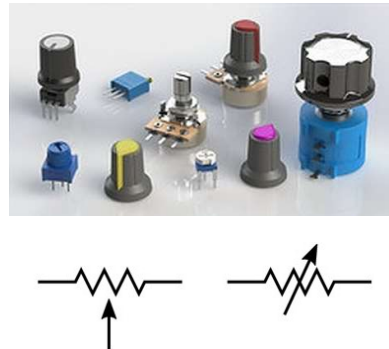


4

4

RESISTOR

- A resistor is a **passive** two-terminal electrical component that implements **electrical resistance** as a circuit element

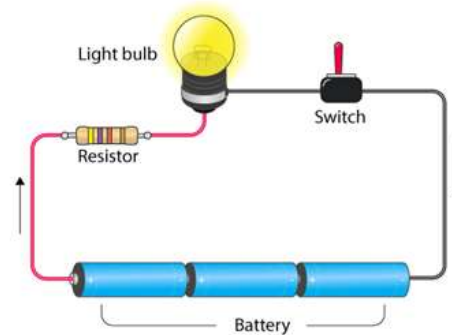- Uses of resistors:
 - To reduce current flow
 - To adjust signal levels
 - To divide voltages
 - To bias active elements
 - To terminate transmission lines



5

5

RESISTOR COLOR CODE

- 4-Band-Code Example

- 1st band = **Green** → 5
 - 2nd band = **Blue** → 6
 - 3rd band = **Yellow** → 10KΩ
 - 4th band = **Gold** → ±5%
- 56x10KΩ ±5%
 ▪ = 560KΩ ±5%

4-Band-Code

2%, 5%, 10% 560k Ω ± 5%

COLOR	1 ST BAND	2 ND BAND	3 RD BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	1Ω	
Brown	1	1	1	10Ω	± 1% (F)
Red	2	2	2	100Ω	± 2% (G)
Orange	3	3	3	1KΩ	
Yellow	4	4	4	10KΩ	
Green	5	5	5	100KΩ	± 0.5% (D)
Blue	6	6	6	1MΩ	± 0.25% (C)
Violet	7	7	7	10MΩ	± 0.10% (B)
Grey	8	8	8		± 0.05%
White	9	9	9		
Gold				0.1Ω	± 5% (J)
Silver				0.01Ω	± 10% (K)

5-Band-Code

0.1%, 0.25%, 0.5%, 1% 237 Ω ± 1%

6

6

OHM'S LAW

- For purposes of circuit analysis, we refer the current in the resistor to the terminal voltage as:

$$v = iR$$

- v = the voltage in volts
- i = the current in amperes
- R = the resistance in ohms (Ω)



7

CONDUCTANCE

- The reciprocal of the resistance is referred to as conductance.

$$G = \frac{1}{R}$$

- G = the conductance in siemens (S)
- R = the resistance in ohms



8

POWER IN A RESISTOR

- Power:

$$p = vi$$

- Power in terms of current:

$$p = i^2 R$$



- Power in terms of voltage:

$$p = \frac{v^2}{R}$$

9

9

INDUCTOR

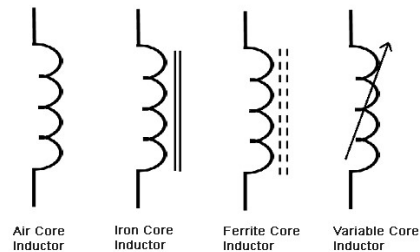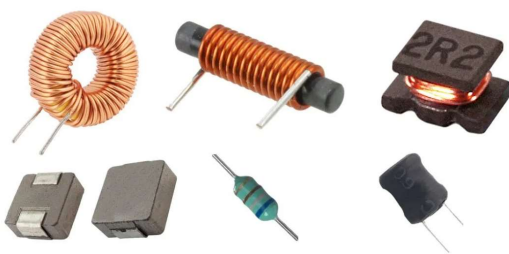

10

10


INDUCTOR

- **Inductance** is the circuit parameter used to describe an inductor.
- Inductance
 - is symbolized by the letter **L**,
 - is measured in **henrys (H)**,
 - is represented graphically as a **coiled wire**, and
 - is a consequence of a **conductor** linking a **magnetic field**.

11

11

SYMBOLS OF INDUCTORS

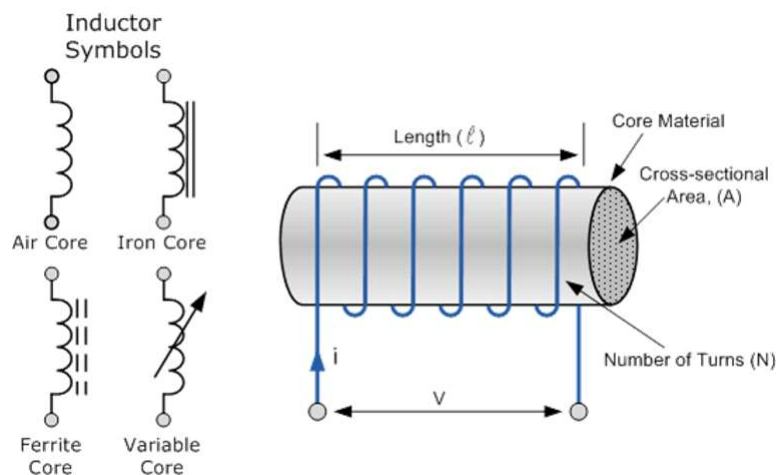


12

12

INDUCTOR V-I EQUATION

$$v = L \frac{di}{dt}$$

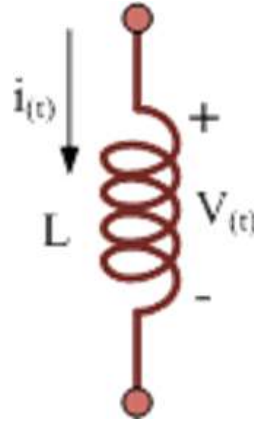- The current reference is in the direction of the voltage drop across the inductor.
 - v is measured in volts
 - L in henrys
 - i in amperes
 - t in seconds



13

13

INDUCTOR I-V EQUATION

$$i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

- $i(t)$ is the current corresponding to t ,
- $i(t_0)$ is the value of the inductor current when we initiate the integration

14

14

INDUCTOR POWER EQUATION

- Power in an inductor:

$$p = vi$$


$$= iL \frac{di}{dt}$$

15

15

INDUCTORS IN SERIES

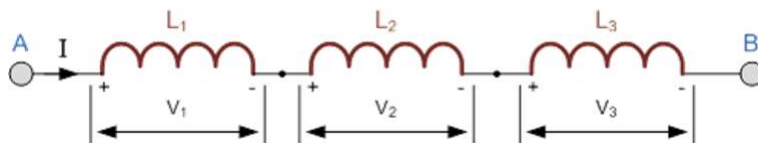- Inductors in series are added together because the number of coil turns is effectively increased, with the total circuit inductance L_T being equal to the sum of all the individual inductances added together.



16

16

INDUCTORS IN SERIES

- Inductors in series have a common current, I , flowing through them:
- $I_{L1} = I_{L2} = I_{L3} = I_{AB}$
- So the total inductance is given as:


$$L_T \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + L_3 \frac{di}{dt}$$

17

17

INDUCTORS IN PARALLEL

- $V_{L1} = V_{L2} = V_{L3} = V_{AB}$

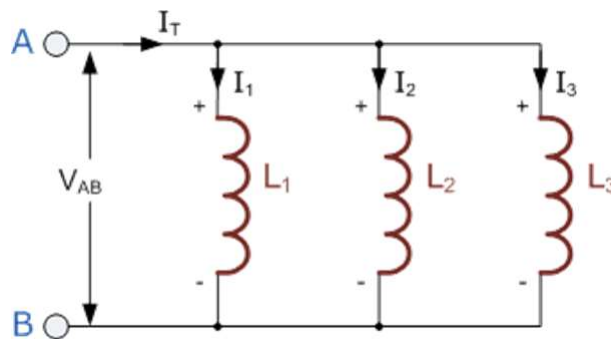

18

18

PARALLEL INDUCTANCE


- The total inductance L_T for N inductors in parallel.

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots + \frac{1}{L_N}$$


19

19

CAPACITOR

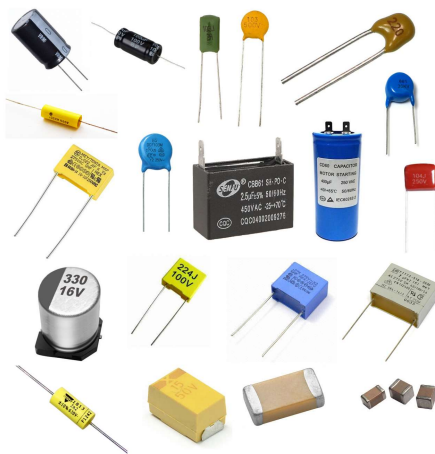

© www.powerelectronicstalks.com

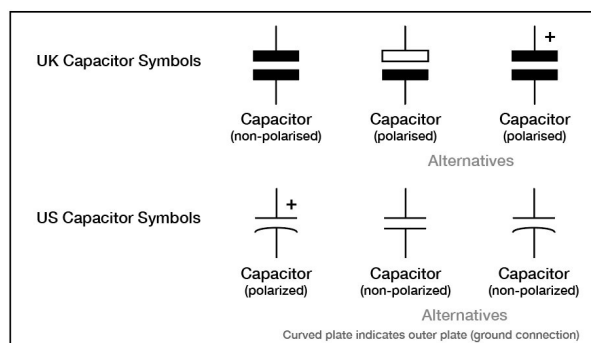


20

20

CAPACITOR CONSTRUCTION AND SYMBOL

- Capacitor, sometimes referred to as a Condenser, is a passive device, and one which **stores its energy** in the form of an electrostatic field producing a potential difference (Static Voltage) across its plates.
- In its basic form a capacitor consists of two or more parallel conductive (metal) plates that do not touch or are connected but are **electrically separated** either by air or by some form of insulating material such as paper, mica or ceramic called the **Dielectric**.

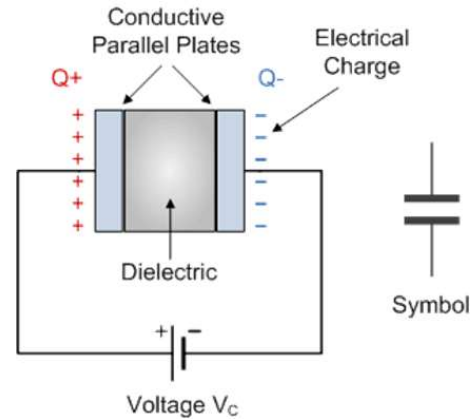

21

21

CHARGE ON A CAPACITOR

- Capacitors can store the electrical charge (Q) between its plates is proportional to the applied voltage, V for a capacitor of known capacitance in Farads.

$$Q = C \times V \text{ Coulombs}$$

- The actual charge Q on the plates of the capacitor and can be calculated as:

$$C = \frac{Q}{V} \text{ or } V = \frac{Q}{C}$$

22

22

DISPLACEMENT CURRENT

- As the voltage varies with time, the displacement of charge also varies with time, causing what is known as the **displacement current**.
- The **current** is proportional to the rate at which the voltage across the capacitor varies with time.

$$i = C \frac{dv}{dt}$$

23

23

CAPACITOR V-I EQUATION

- Carrying out the integration of both sides, we have:

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

24

24

CAPACITOR POWER EQUATION

- We can derive the power relationship for the capacitor.

$$p = vi$$


$$= vC \frac{dv}{dt}$$

25

25

CAPACITORS IN PARALLEL

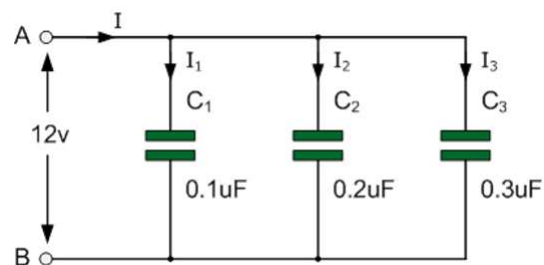- Capacitors in Parallel have a common voltage supply across them giving
- $V_{C1} = V_{C2} = V_{C3} = V_{AB}$



26

26

CAPACITORS IN PARALLEL

- Based on the above circuit, we have

$$i_1 = C_1 \frac{dv}{dt}, \quad i_2 = C_2 \frac{dv}{dt}, \quad i_3 = C_3 \frac{dv}{dt}$$

$$i_T = i_1 + i_2 + i_3$$


$$\therefore i_T = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + C_3 \frac{dv}{dt}$$

$$i_T = (C_1 + C_2 + C_3) \frac{dv}{dt}$$

27

27

CAPACITORS IN PARALLEL

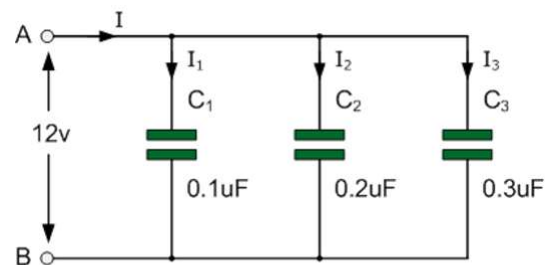


$$C_T = C_1 + C_2 + C_3 + \dots \text{etc}$$

28

28

CAPACITORS IN SERIES

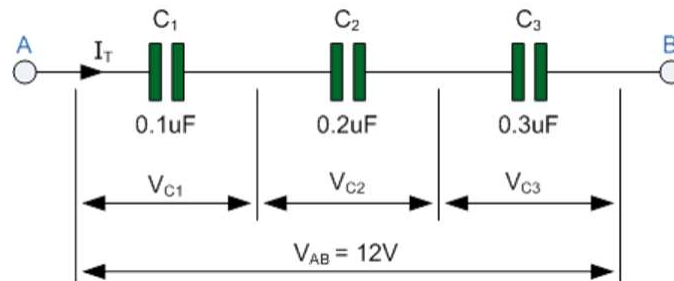- When capacitors are in series, the charging current flowing through the capacitors is the same for all capacitors as it only has one path to follow and $i_T = i_1 = i_2 = i_3$ etc



29

29

CAPACITORS IN SERIES

- Capacitors in series all have the same current so each capacitor stores the same amount of charge regardless of its capacitance.
- $Q_T = Q_1 = Q_2 = Q_3$

$$V_{AB} = V_{C1} + V_{C2} + V_{C3} = 12\text{V}$$

$$V_{C1} = \frac{Q_T}{C_1}, V_{C2} = \frac{Q_T}{C_2}, V_{C3} = \frac{Q_T}{C_3}$$

30

30

CAPACITORS IN SERIES

- The total value for capacitors in series equals the reciprocal of the sum of the reciprocals of the individual capacitances.

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \text{etc}$$

31

31

KIRCHHOFF'S LAWS

32

32

KIRCHHOFF'S LAWS


- A circuit is said to be solved when the voltage across and the current in every element have been determined.
- Ohm's law is an important equation for deriving such solutions.
- However, Ohm's law may not be enough to provide a complete solution.

33

33

KIRCHHOFF'S CURRENT LAW (KCL)

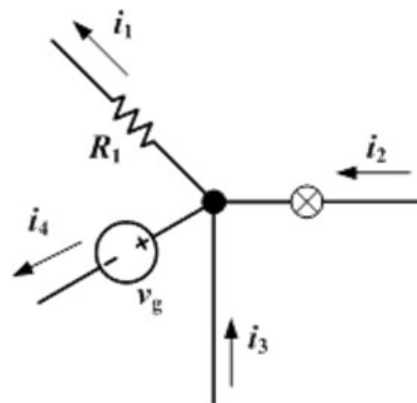- Kirchhoff's Current Law (KCL) states that the algebraic sum of all the currents at any node in a circuit equals zero.
- For example in the figure, $i_1 - i_2 - i_3 + i_4 = 0$




34

34

KIRCHHOFF'S VOLTAGE LAW (KVL)

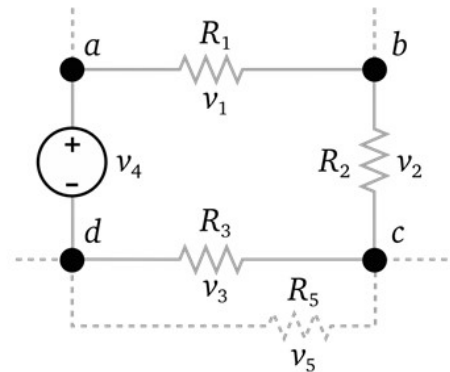- Kirchhoff's Voltage Law (KVL) states that the algebraic sum of all the voltages around any closed path in a circuit equals zero.
- For example in the figure, $v_1 + v_2 + v_3 + v_4 = 0$




35

35

CLOSED PATH

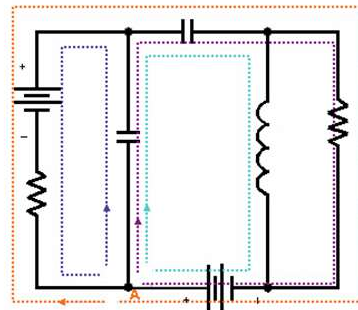- A closed path is also called a loop.
- Starting at an arbitrarily selected node, we trace a closed path in a circuit through selected basic circuit elements and return to the original node without passing through any intermediate node more than once.



36

36

ANY QUESTIONS ?

37