


Homework 1: Circuit Analysis and Operational Amplifier

Submission Instructions:

- Answer all the questions **with clear steps**.
- Save your answers in **pdf** file
- Upload the pdf file to **Blackboard** before the deadline stated in Blackboard
- Marks will be deducted for late submission, deduct 10 marks per every 1-hour interval (e.g. deduct 20 marks for 61 minutes late).


1. Given the following voltage divider circuit with $V_{in}=12V$, $V_{out}=3V$, and $Z_1=450k\Omega$. What is the resistance of Z_2 ?

[10 marks]

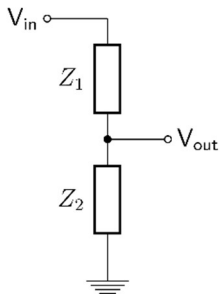

2. Given the following capacitor network. What is the total capacitance between A and B?

[10 marks]

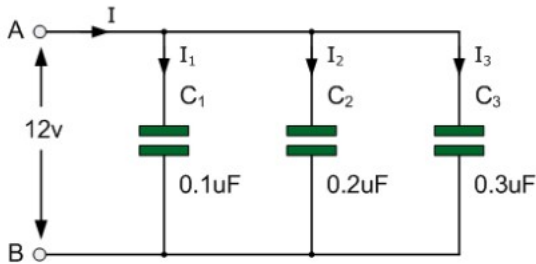


3. If the AC voltage across an inductor is $5\cos(2000t)V$ and the inductance of the inductor is $5\mu H$. Assume the initial current $I_0=0A$, what is the current going through the inductor at time t ?


[10 marks]

4. Given the following resistor network. What are the total current (i.e. I_{total}) and the currents going through each resistor (i.e. I_{R1} , I_{R2} , and I_{R3})?

[20 marks]

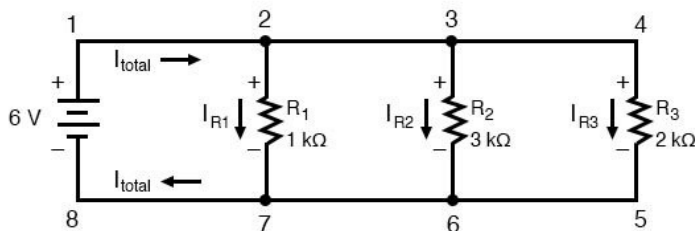


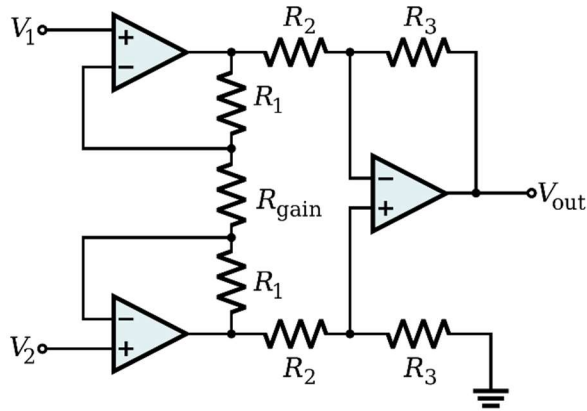5. Given the following instrumentation amplifier and its gain (A_v) as below. Prove the given gain equation with clear steps. [20 marks]



$$A_v = \frac{V_{out}}{V_2 - V_1} = \left(1 + \frac{2R_1}{R_{gain}} \right) \frac{R_3}{R_2}$$

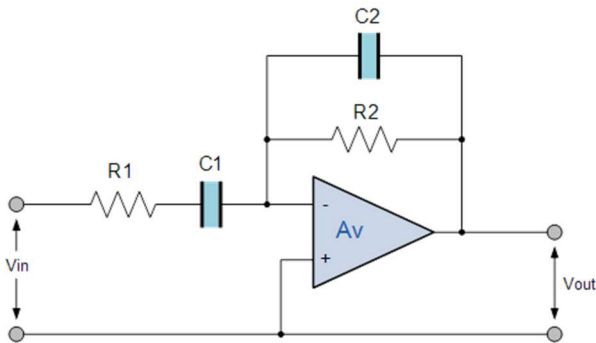6. Given the following active inverting band pass filter circuit with $C1=100\text{nF}$, $C2=1\text{nF}$, $R1=1.6\text{k}\Omega$, and $R2=80\text{k}\Omega$. What are the cut-off frequencies (i.e. f_{c1} and f_{c2}) and the voltage gain (A_v)? [15 marks]



7. Can the filter circuit in Question 6 filter out 100Hz noise? Explain briefly. [15 marks]

THE END