


#### Lab 4: Basic Circuit Analysis

##### Submission Instructions:

- Save all the circuit files in .TSC, which you created in the lab
- Answer all the questions in the .docx answer sheet
- Compress all the above files to one single .zip file
- Upload the .zip file before the deadline stated in Blackboard
- Marks will be deducted for late submission, deduct 10 marks per every 10-minute interval (e.g. deduct 20 marks for 11 minutes late).
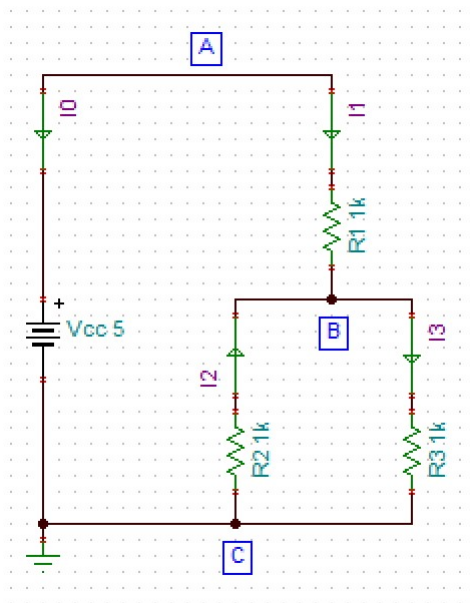
### 1. KVL and KCL

Construct the following resistive circuit using TINA. It consists of 5V **Battery**, 1k ohm **Resistors**, and **Current Arrows** which define the directions of the currents,  $I_0$ ,  $I_1$ ,  $I_2$ , and  $I_3$ .




Select **Analysis: DC Analysis: Table of DC results**. Determine the results of the following measurement according to the content of the table.

Voltages/Currents	
I_R1[6.5]	3.33mA
I_R2[2.0]	1.67mA
I_R3[3.0]	1.67mA
I0	-3.33mA
I1	3.33mA
I2	-1.67mA
I3	1.67mA
V_J[4.1]	0V
V_J1[4.6]	0V
V_J2[2.5]	0V
V_J3[5.3]	0V
V_R1[6.5]	3.33V
V_R2[2.0]	1.67V
V_R3[3.0]	1.67V
V_Vcc[1.0]	5V
VP_1	5V
VP_2	1.67V
VP_3	1.67V
VP_4	5V
VP_5	1.67V
VP_6	5V
Show	
<input checked="" type="checkbox"/> Nodal Voltages	<input checked="" type="checkbox"/> Currents
<input checked="" type="checkbox"/> Other Voltages	<input checked="" type="checkbox"/> Outputs
<input type="button" value="Cancel"/>	<input type="button" value="Help"/> <input type="button" value="Print"/>


- a. Voltage measurement
  - i. Measure the absolute value of voltage  $V_{cc}$  across the nodes A and C
  - ii. Measure the absolute values of voltages  $V_1$  across  $R_1$ ,  $V_2$  across  $R_2$ , and  $V_3$  across  $R_3$
  - iii. **Write down the absolute values of the voltages on the answer sheet**
  - iv. **Write down an equation of  $V_{cc}$  in terms of  $V_1$ ,  $V_2$ , and/or  $V_3$**
- b. Current measurement
  - i. Measure the currents  $I_0$ ,  $I_1$ ,  $I_2$ , and  $I_3$  according to the current flow directions as defined in the circuit diagram
  - ii. **Write down the currents on the answer sheet**
  - iii. **Write down an equation of  $I_0$  in terms of  $I_1$**
  - iv. **Write down an equation of  $I_1$  in terms of  $I_2$  and  $I_3$**
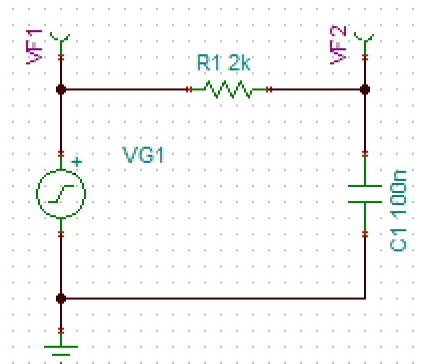
## 2. Passive Low Pass Filter

Construct a first order Low Pass Filter (LPF) as shown below, where  $R_1 = 2\text{k}\Omega$ , and  $C = 0.1\mu\text{F} = 100\text{nF}$ .




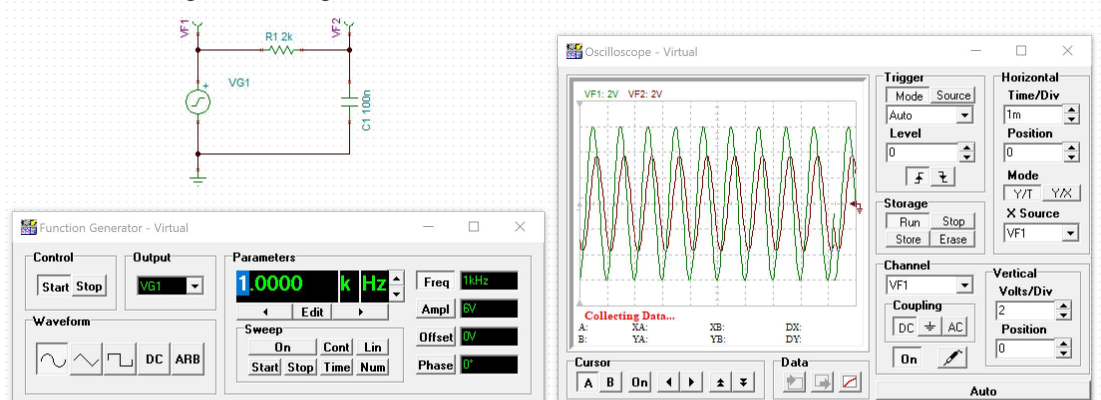- a. Frequency Response
  - i. To observe the frequency response of the circuit, inject a sine wave at  $VG_1$  using Function Generator, and check both input  $VF_1$  and output  $VF_2$  using Oscilloscope
    1. Use the function generator to generate a 6V, 1kHz, sine wave



2. Use the Oscilloscope to monitor both  $VF_1$  and  $VF_2$ . At **Channel**, turn both  $VF_1$  and  $VF_2$  **On**. By adjusting Horizontal (1m s./Div) and Vertical (2 V/Div) scales, you should be able to display two sine waves as shown above. As you can see, when the input is at 1kHz, the output amplitude is reduced from 6V to less than 4V.

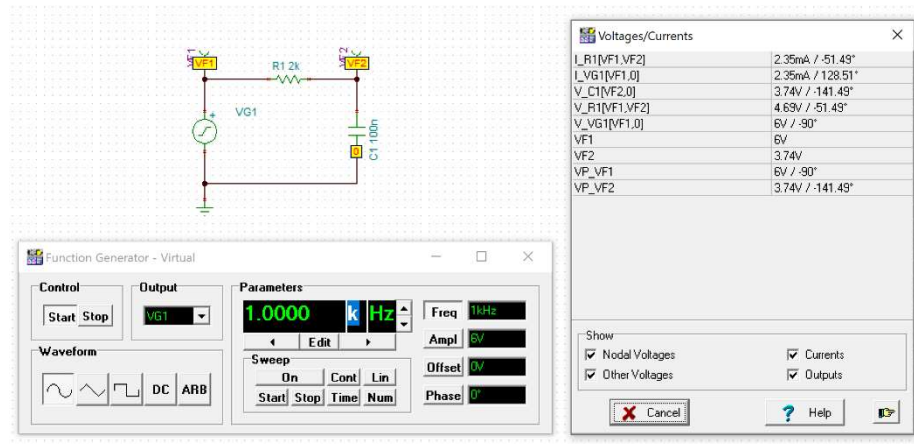3. To observe the output amplitude precisely, we can use **Analysis: AC Analysis** to observe the output voltage **VP\_VF2 = 3.74V** instead of using oscilloscope.



4. By changing the frequency of **VG1** according to the table in the answer sheet, and measuring the output voltage **VP\_VF2**, we can plot a graph of the frequency response of the circuit
- ii. Cut-off Frequency
    1. By calculation, what is the cut-off frequency,  $f_c$ , of the LPF?
    2. Based on the graph in part iii below, what is the output voltage of **VF2** at  $f_c$ ? [Plot the graph before you answer this question]
  - iii. **Write down the collected data, and plot the frequency response of the circuit on the answer sheet**

The Chinese University of Hong Kong  
Department of Computer Science and Engineering  
CENG2030 Fundamentals of Embedded System Design

Lab 4: Basic Circuit Analysis

Answer Sheet

Student Name: \_\_\_\_\_

SID: \_\_\_\_\_

**1. KVL and KCL [54%]**

a. Create and upload the TSC circuit file. [10%]

b. Voltage measurement

Vcc: \_\_\_\_\_ [4%]

V1: \_\_\_\_\_ [4%]

V2: \_\_\_\_\_ [4%]

V3: \_\_\_\_\_ [4%]

Equation: Vcc = \_\_\_\_\_ [4%]

c. Current measurement

I0: \_\_\_\_\_ [4%]

I1: \_\_\_\_\_ [4%]

I2: \_\_\_\_\_ [4%]

I3: \_\_\_\_\_ [4%]

Equation: I0 = \_\_\_\_\_ [4%]

Equation: I1 = \_\_\_\_\_ [4%]

2. Passive Low Pass Filter

[46%]

- a. Create and upload your circuit in TSC file.
- b. Frequency Response
- [10%]

- i. Collected Data
- [12%]

Frequency of Vin (Hz)	50	100	200	500	1k	2k	5k	10k	20k	50k	100k	200k
Vpp of Vout (V)												

- i. Cut-off Frequency
- fc:  $fc = \frac{1}{2\pi CR}$  = \_\_\_\_\_
- [4%]
- Vout at fc: \_\_\_\_\_
- [4%]

- ii. Graph Plotting
- [16%]

