

CENG2030 FUNDAMENTALS OF EMBEDDED SYSTEM DESIGN

LECTURE 9: SENSOR AND ACTUATOR

By Dr. Anthony Sum
Department of Computer Science and Engineering
The Chinese University of Hong Kong



1

CONTENTS

- Common Sensors
 - IR Sensor
 - Ultrasound Sensor
 - Photoresistor
 - LIDAR
 - IMU
- Common Actuators
 - D.C. Motor
 - Servo Motor




2

IR SENSOR

Transmitter (Infrared light emitter diode, LED)

Receiver (Infrared photodiode, PD)

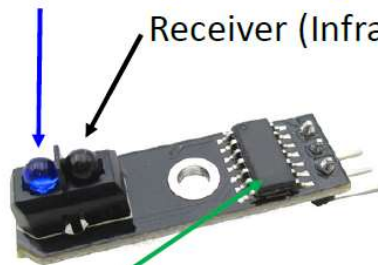


Lower-cost model uses logic IC to determine the logic low and high.

3

3

IR REFLECTIVE SENSOR

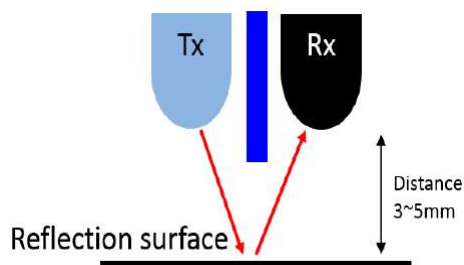


- The reflected light intensity depends on:
 - The **reflectivity** of the surface
 - The **distance**
- “**White**” surface reflects more light than “**Black**” or empty space

4

4

IR SENSOR IN ACTION

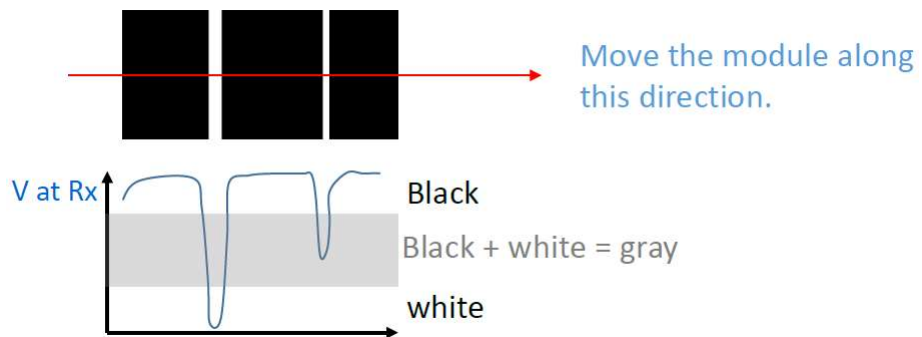

5

5


LONG RANGE IR SENSOR



6

6

ULTRASOUND SENSOR

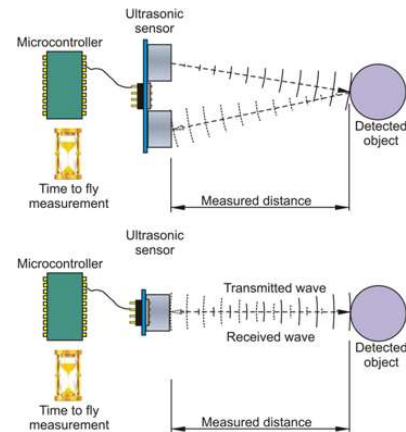

7

7


ULTRASOUND SENSOR

- An ultrasonic sensor is an instrument that measures the **distance** to an object using ultrasonic sound waves.
- An ultrasonic sensor uses a transducer to **send** and **receive ultrasonic pulses** that relay back information about an object's proximity.
- High-frequency sound waves reflect from boundaries to produce distinct echo patterns.

8

8


APPLICATION OF ULTRASOUND SENSOR

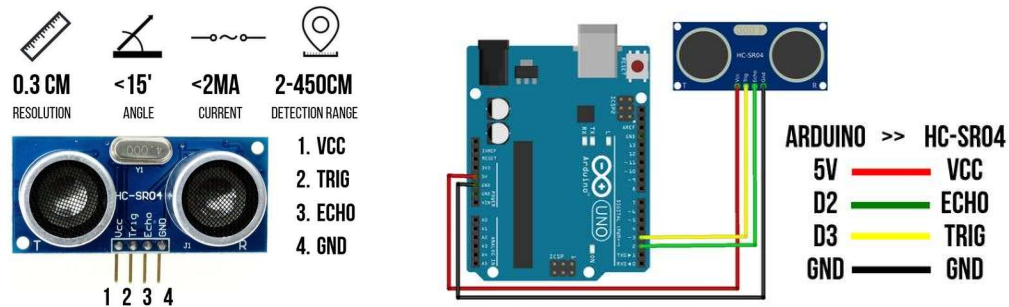

9

9


APPLICATION OF ULTRASOUND SENSOR

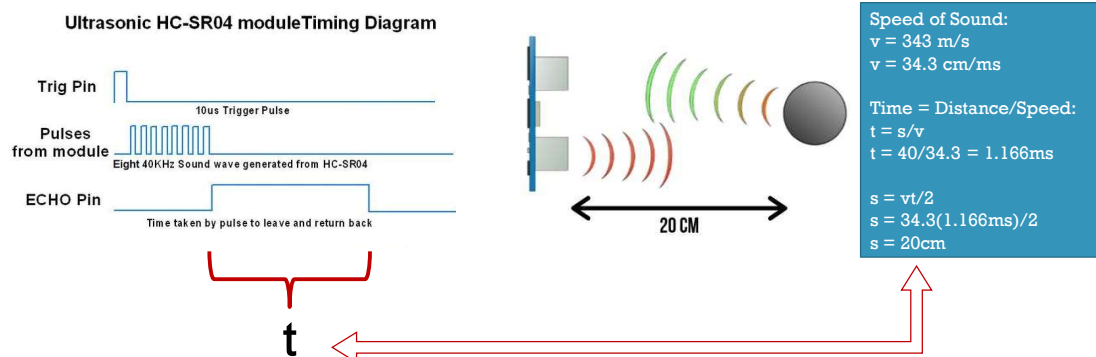

10

10

PHOTORESISTOR

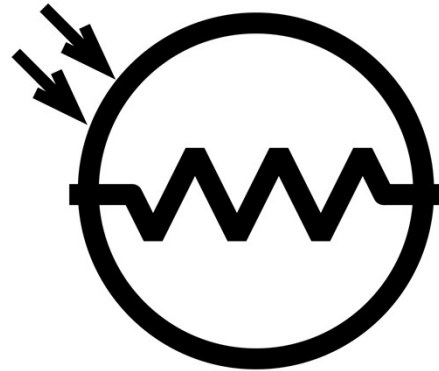


11

11

PHOTORESISTOR

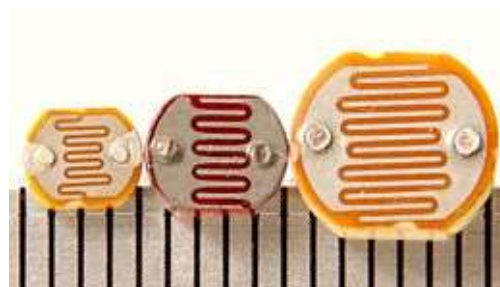
- Photoresistor is also called
 - Light Decreasing Resistance (LDR)
 - Light-dependent resistor
 - Photo-conductive cell
- Photoresistor is a passive component that **decreases resistance** with respect to receiving luminosity (light) on the component's sensitive surface.



12

12

SAMPLE CIRCUIT OF LDR

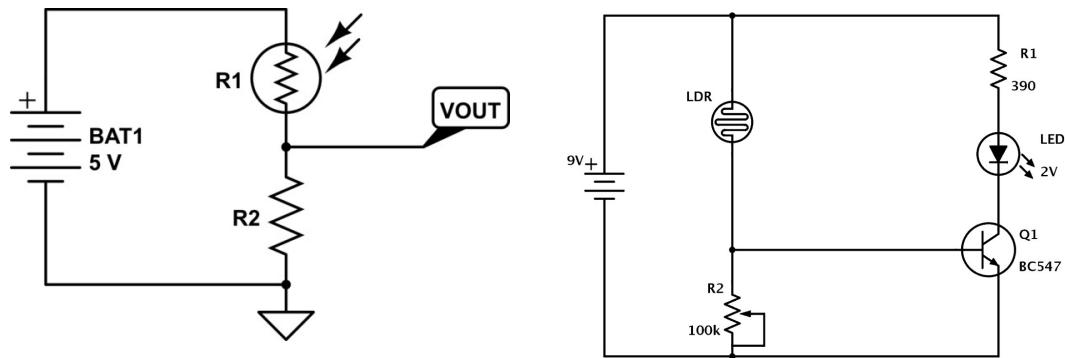


13

13

ARDUINO WITH LDR

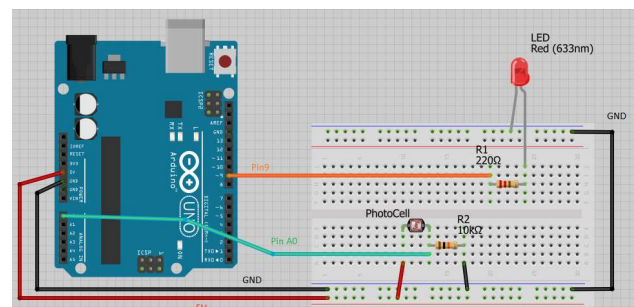- The output pin of the LDR circuit is connected to the A0 of Arduino UNO board
- A0 is one of the analog input pin



14

14

ARDUINO WITH LDR

```
// IO Ports
const int pResistor = A0;
const int ledPin = 9;

//Photoresistor value from 0 to 1023
int value;

void setup(){
  pinMode(ledPin, OUTPUT);
  pinMode(pResistor, INPUT);
}
```

```
void loop(){
  value = analogRead(pResistor);



  //You can change value "25"
  if (value > 25){
    //Turn led off
    digitalWrite(ledPin, LOW); }
  else{
    //Turn led on
    digitalWrite(ledPin, HIGH); }

  delay(500);
}
```

15

15

IMU

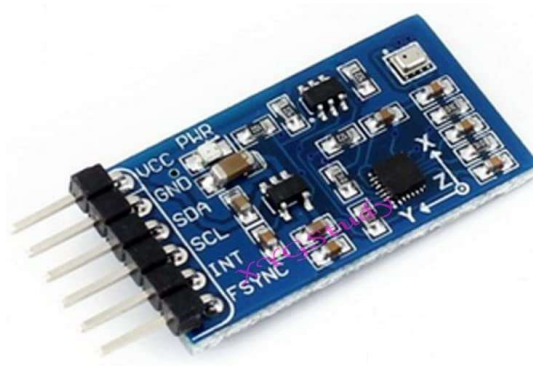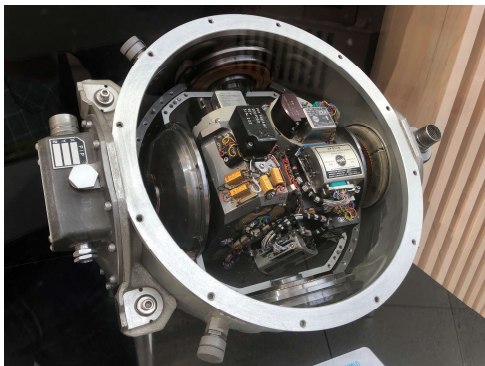


16

16

IMU

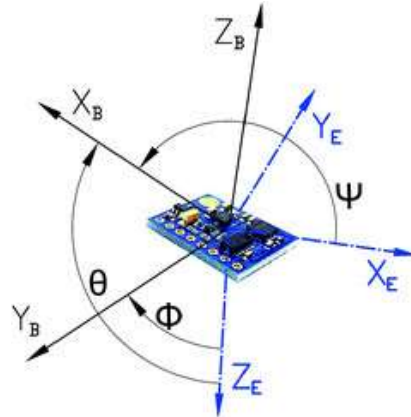- IMU stands for **Inertial Measurement Unit**
- IMU contains sensors such as **accelerometers**, **gyroscopes**, and **magnetometers**
 - Accelerometer measures velocity and acceleration
 - Gyroscope measures rotation and rotational rate
 - Magnetometer establishes cardinal direction (directional heading)



17

17

APPLICATIONS OF IMU

- Navigation
 - Manned and unmanned aircraft: IMU's measurements to calculate altitude and relative position to a reference frame, making them exceedingly useful in aircraft applications.
 - GPS positioning systems: IMUs serve as a supplement to GPS positioning systems, allowing the navigational device to continue with an estimated position and heading if it loses satellite connection.




18

18

APPLICATIONS OF IMU

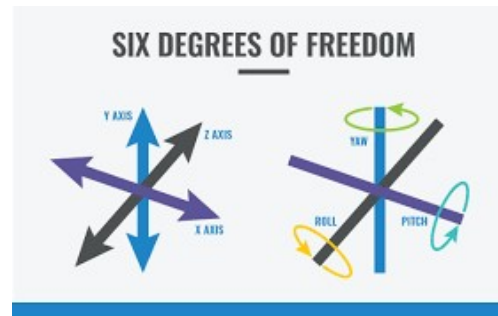- Motion detection
 - Most smartphones, tablets and fitness tracking devices contain a low-cost IMU
 - IMUs are involved in sports training applications that need to measure, for example, the precise angle and force of a swing in golf or baseball.
 - IMUs drive the self-balancing systems of personal transportation devices like Segways and hoverboards.



19

19

DISADVANTAGES OF IMU

- The principal disadvantage of an IMU is that they are prone to **error** that **accumulates over time**, also known as “**drift**.”
 - Because the device is always measuring **changes relative to itself**, the IMU constantly rounds off small fractions in its calculations, which accumulate over time. Left uncorrected, these tiny imprecisions can add up to significant errors.
- Still, when coupled with a corrective technology or a human operator, IMUs can be a beneficial supplement to other sensors. In precision applications, you can suspend the sensors from shock absorbers to mitigate errors as well as protect the unit.

20

20

ACTUATOR

21

21

DC MOTOR





22

22

DC MOTOR WORKING PRINCIPLE

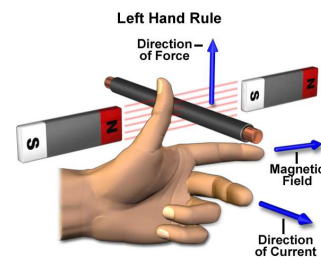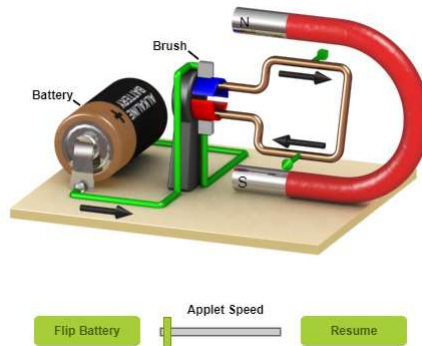- Online simulator of DC motor [Source: MagLab]
 - <https://nationalmaglab.org/education/magnet-academy/watch-play/interactive/dc-motor>



23

23


SERVO MOTOR



24

24

SERVO MOTOR BY PWM

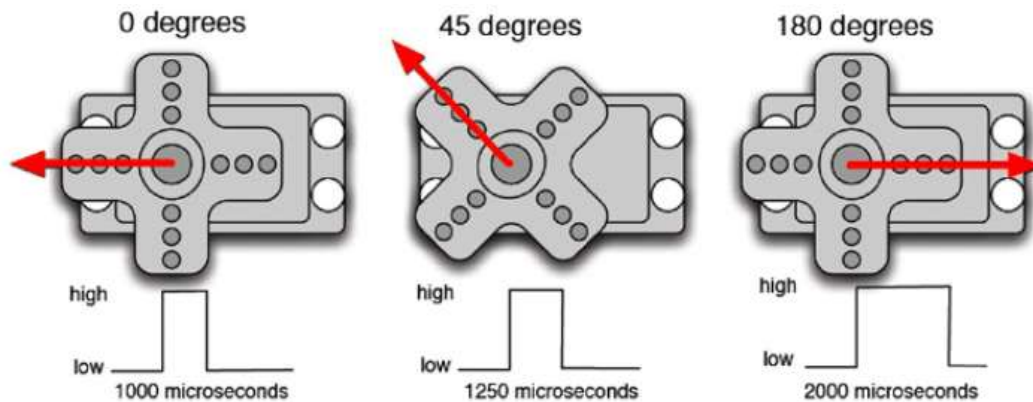


25

25

ARDUINO WITH SERVO

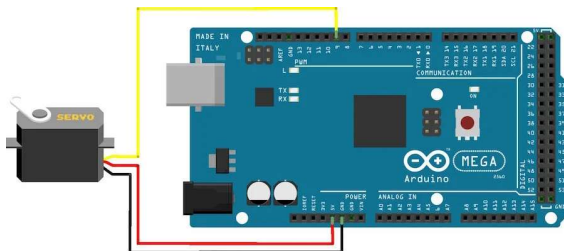- There are normally 3 pins on a servo motor
 - Vcc for 5V
 - GND for Ground
 - PWM for Pulse Width Modulated signal
- PWM pin is connected to one of the **digital output** pin of Arduino



26

26

ARDUINO WITH SERVO

```
#include <Servo.h>

Servo myservo;

int angle=0;

void setup()
{
  // attach servo at pin 9
  myservo.attach(9);
}
```

Note: For Arduino Uno, Nano, & Mini, only Pin 3, 5, 6, 9, 10, & 11 can be used for PWM output.

```
void loop()
{
  for(angle=0; angle<180; angle+=1)
  {
    myservo.write(angle);
    delay(15);
  }

  delay(1000);

  for(angle=180; angle>0; angle-=5)
  {
    myservo.write(angle);
    delay(5);
  }

  delay(1000);
}
```

27

27

ANY QUESTIONS ?

28

28